

## Complex Impedance

For any circuit component, there will be current  $i(t)$  and a voltage  $v(t)$ , they will oscillate at the same frequency.

The impedance of a component is the complex equivalent of resistance.

$$\tilde{Z} = \frac{\tilde{V}}{\tilde{I}}$$

Inductor:

$$\begin{aligned} i &= I_0 \cos(\omega t) && \left. \begin{array}{l} \text{AC current} \\ \text{AC voltage} \end{array} \right\} \\ v_L &= L \frac{di}{dt} = -I_0 \omega L \sin \omega t \\ &= I_0 \omega L \cos(\omega t + \pi/2) \end{aligned}$$

Scaled by  $\omega L$   $\nearrow$  phase difference of  $\pi/2$

at the time  $t=0$ ,

$$\begin{aligned} \tilde{I} &= I_0 e^{j\omega t} = I_0 e^{j\omega 0} = I_0 \\ \tilde{V}_L &= I_0 \omega L e^{j(\omega t + \pi/2)} = I_0 \omega L e^{j\pi/2} \end{aligned}$$

$$\tilde{Z}_L = \frac{\tilde{V}_L}{\tilde{I}} = \omega L e^{j\pi/2} = j\omega L$$

Capacitor:

$$\begin{aligned} v_C &= V_0 \cos(\omega t) \\ i &= C \frac{dv_C}{dt} = -V_0 C \sin(\omega t) \\ &= V_0 C \cos(\omega t + \pi/2) \end{aligned}$$

amplitude shifted by  $C$   $\nearrow$  phase shift of  $2\pi$ .

$$\tilde{V}_C = V_0 e^{j(\omega t)}$$

$$\tilde{I} = V_0 \omega C e^{j(\omega t + \pi/2)}$$

$$\tilde{Z}_C = \frac{\tilde{V}_C}{\tilde{I}} = \frac{V_0 e^{j\omega t}}{V_0 \omega C e^{j\omega t} e^{j\pi/2}} = \frac{1}{j\omega C}$$

$$= \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

Resistor:

$$\tilde{V}_R = V_0 e^{j\omega t}$$

$$\tilde{I} = \frac{\tilde{V}_R}{R} = \frac{V_0}{R} e^{j\omega t}$$

$$\tilde{Z} = \frac{\tilde{V}_R}{\tilde{I}} = \frac{V_0}{V_0/R} = R$$

## Equivalent Impedance

Series:

$$\tilde{Z}_T = \tilde{Z}_1 + \tilde{Z}_2 + \dots$$

Parallel:

$$\frac{1}{\tilde{Z}_T} = \frac{1}{\tilde{Z}_1} + \frac{1}{\tilde{Z}_2} + \dots$$

## AC Analysis

All potential differences & currents will oscillate at the same frequency.


The phase difference between the voltage & current can be found by  $\arg(\tilde{Z})$ . The absolute value is the ratio of the amplitudes.

$$|\tilde{Z}| = \frac{|\tilde{V}|}{|\tilde{I}|}$$
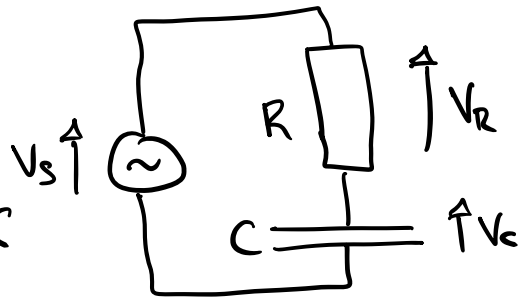
## Series RC Circuit

$$\text{KVL: } \tilde{V}_S = \tilde{V}_R + \tilde{V}_C$$

When we have an idealised AC voltage source, we can use



$$V_S(t) = V_0 \cos(\omega t + \phi)$$

As this signal exists for all time, there are no transient effects, we're only looking at the steady-state effects.

The circuit impedance is 
$$\tilde{Z} = \tilde{Z}_R + \tilde{Z}_C = R - j\omega C$$

$$\tilde{I} = \frac{\tilde{V}_S}{\tilde{Z}}$$

$$\tilde{V}_C = \tilde{I} \tilde{Z}_C = \frac{\tilde{V}_S}{\tilde{Z}_R + \tilde{Z}_C} \tilde{Z}_C = \underbrace{\frac{\tilde{Z}_C}{\tilde{Z}_R + \tilde{Z}_C}}_{\text{impedance divider}} \tilde{V}_S$$

$$\tilde{V}_C = \tilde{V}_S \times \frac{-j/\omega C}{R - j\omega C}$$

$$\tilde{V}_R = \tilde{V}_S - \tilde{V}_C$$