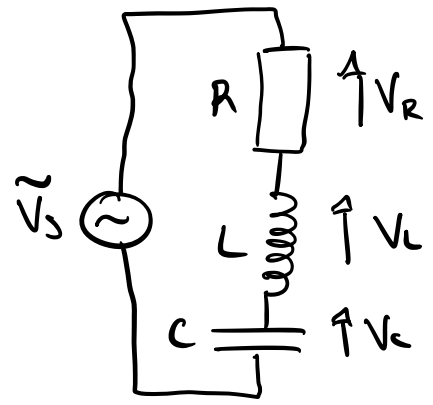


# Series LCR Circuit

$$V_s = V_0 \cos(\omega t)$$

$$\tilde{V}_s = V_0 \quad (\text{Re}\{\tilde{V}_s e^{j\omega t}\} = V_0 \cos(\omega t))$$



$$\tilde{Z} = \tilde{Z}_R + \tilde{Z}_L + \tilde{Z}_C = R + j\omega L - \frac{j}{\omega C}$$

$$\tilde{I} = \frac{\tilde{V}}{\tilde{Z}} = I_0 e^{j\phi}$$

$$I_0 = \frac{V_0}{\sqrt{\tilde{Z} \tilde{Z}^*}} = \frac{V_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

$$\tan \phi = \frac{-(\omega L - 1/\omega C)}{R}$$

(Steady state solution, no transient effects)

$$\tilde{V}_C = \tilde{I} \tilde{Z}_C \quad \tilde{V}_R = \tilde{I} R$$


Resonance:

Occurs when  $\omega = \omega_0$ .

$$\tilde{Z}_C = -\tilde{Z}_L \Rightarrow \tilde{Z} = R$$

$$I = V_0/R \quad \phi = 0$$

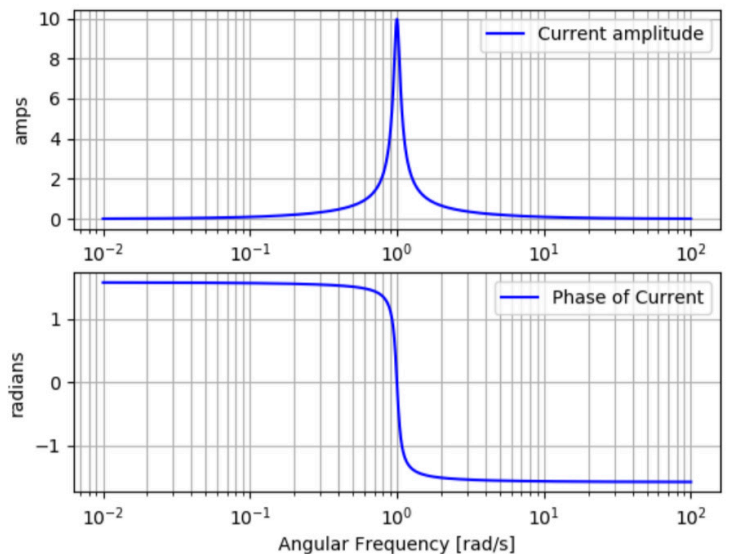Max power! At resonance,  
 $(\omega L - 1/\omega C) = 0 \Rightarrow \omega_0 = 1/\sqrt{LC}$



$$P_R(t) = V_R i = i^2 R = I_0^2 \cos^2(\omega t + \phi) R$$

$$P_{avg} = \langle P_R(t) \rangle = \frac{I_0^2 R}{2} \quad (\langle \cos^2(x) \rangle = 1/2)$$

## Bandwidth

Both LC & RL have a single cut off frequency  $\omega_c$ . However an LCR circuit has two cut off frequencies  $\omega_l$  &  $\omega_h$ . The definition is the same: When the power falls to half of the maximum.

We define the bandwidth  $\Delta\omega$  as  $\Delta\omega = \omega_h - \omega_l$ .

$$\Delta\omega = \omega_h - \omega_l = \frac{R}{L} = \gamma$$

## Q Factor

$$Q = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{\gamma}$$

A circuit with a high Q Factor has a narrow peak. It is related to the rate of loss of energy.