


# Damped Harmonic Oscillator

$$V_s = \begin{cases} \mathcal{E}, & t < 0 \\ 0, & t \geq 0 \end{cases}$$

for  $t \geq 0$ :

$$\begin{aligned} 0 &= V_R + V_C + V_L \\ &= iR + \frac{q}{C} + L \frac{di}{dt} \\ &= \frac{q}{C} + R \frac{dq}{dt} + L \frac{d^2q}{dt^2} \end{aligned}$$
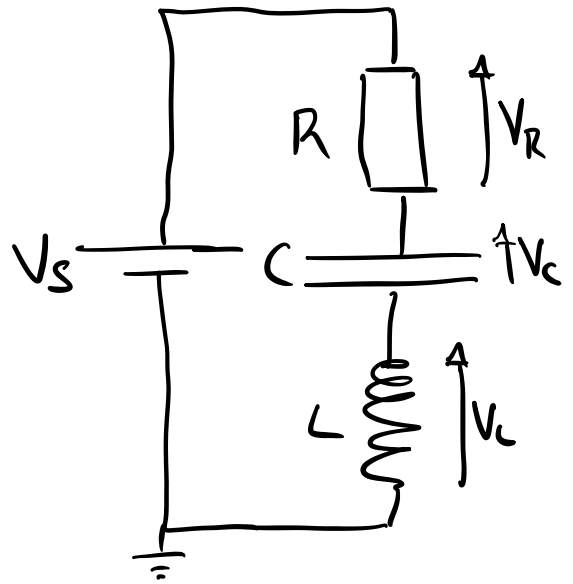
$$\begin{aligned} 0 &= \frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q \\ &= \ddot{q} + \gamma \dot{q} + \omega_0^2 q \end{aligned}$$



$$\gamma = \frac{R}{L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Our initial conditions are:  $V_R = V_L = 0$ ,  $V_C = \mathcal{E}$ .  
The form of our solution depends upon the sign of  $\gamma^2 - 4\omega_0^2$ .

$$\omega_0 > \frac{\gamma}{2}$$

$\Delta$  underdamped  
 $\Delta$  exponential  
decaying oscillation

$$\omega_0 = \frac{\gamma}{2}$$

$\Delta$  critically damped  
 $\Delta$  no oscillation

$$\omega_0 < \frac{\gamma}{2}$$

$\Delta$  overdamped  
 $\Delta$  exponential

We'll mostly explore the underdamped solution but also the critically damped one too.

## Under-Damped Solution ( $\omega_0 > \frac{\gamma}{2}$ )

From complex analysis, we get the solution:



$$q = \frac{q_0 \omega_0}{\omega_d} e^{-\frac{\gamma t}{2}} \cos(\omega_d t + \phi)$$

$q_0$  = initial charge on capacitor  
 $\omega_d$  = damping frequency

$$q_0 = C\mathcal{E}$$

$$\omega_d = \sqrt{\omega_0^2 - \frac{\gamma^2}{4}}$$
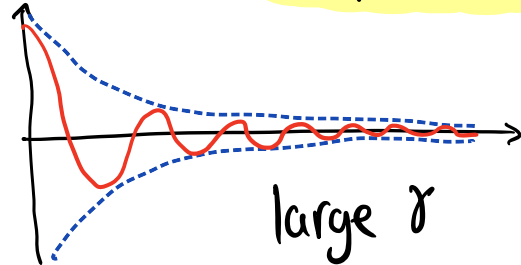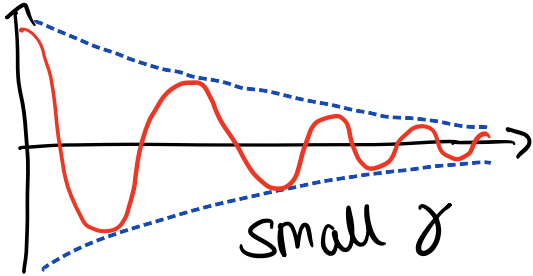
$$\tan \phi = -\frac{\gamma}{2\omega_d}$$



Power

$$\begin{cases} P_R = V\dot{q} = \dot{q}^2 R = \dot{q}^2 R \\ P_L = V\dot{q} = L\ddot{q}\dot{q} = L\dot{q}\ddot{q} \\ P_C = V\dot{q} = \frac{q}{C}\dot{q} = \frac{q\dot{q}}{C} \end{cases}$$


$$(P = I^2 R)$$

$$(P_L = \frac{d}{dt}(\frac{LI^2}{2}))$$


$$(P_C = \frac{d}{dt}(\frac{Q^2}{2C})) \quad (\frac{CV^2}{2} = \frac{Q^2}{2C})$$
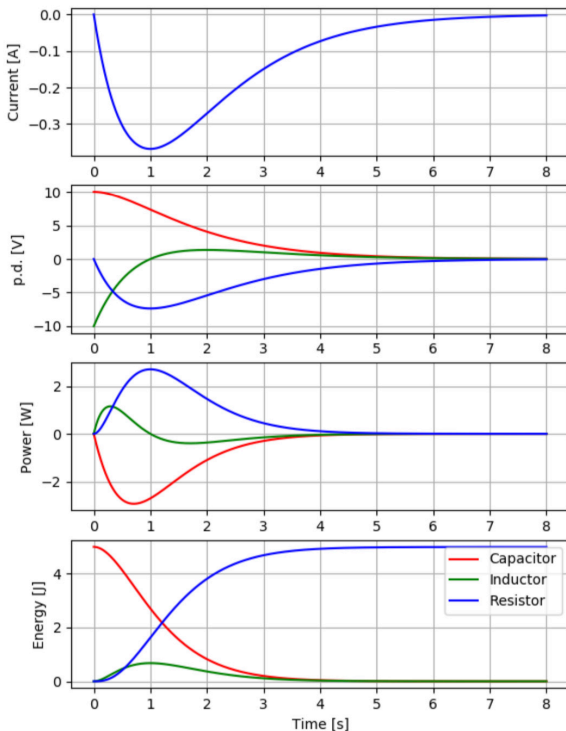
## Critically Damped Solution

$$q = q_0(1 + \frac{\gamma t}{2})e^{-\frac{\gamma t}{2}}$$



under-damped

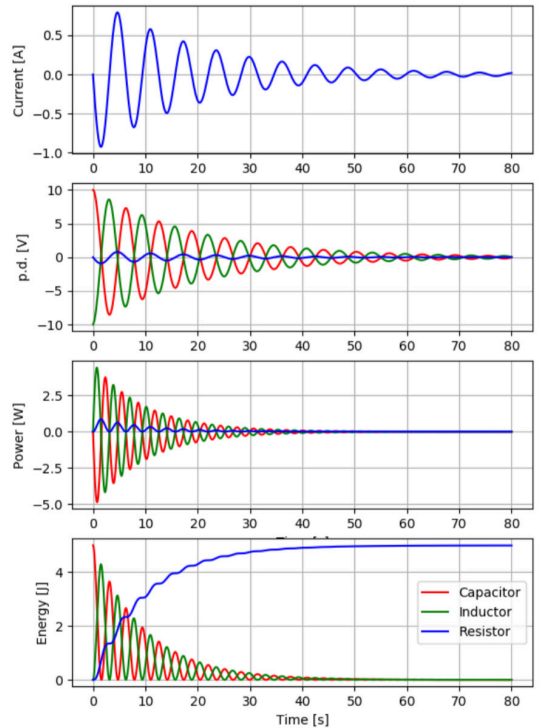

critically damped