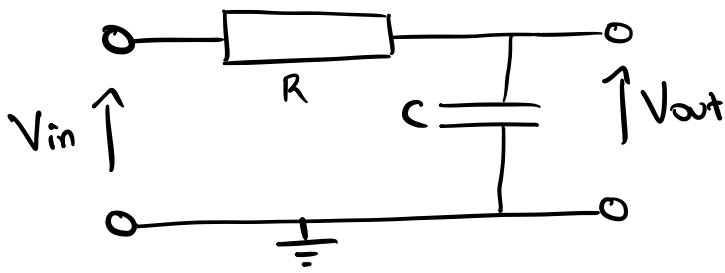


## Low-Pass RC Circuit



- Capacitor impedance depends on frequency.
- Used to filter the noise, remove a range of frequencies from a signal.

$$\begin{aligned}\tilde{V}_{out} &= \tilde{V}_{in} \times \frac{\tilde{Z}_c}{\tilde{Z}_R + \tilde{Z}_c} \\ &= \tilde{V}_{in} \times \frac{-j/\omega C}{R - j/\omega C} = \tilde{V}_{in} \times \frac{1}{1 + j\omega CR}\end{aligned}$$

### Gain

Gain is the output to input ratio. It is complex & shows how the filter changes the amplitude & phase of the input.

$$\tilde{G} = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{1}{1 + j\omega CR} = G e^{j\phi}$$

$$G = |\tilde{G}| = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}} = \frac{|\tilde{V}_{out}|}{|\tilde{V}_{in}|}$$


$$\phi = \arg(\tilde{G}) = -\tan^{-1}(\omega CR)$$

The magnitude of gain is often given in decibels.

$$G_{dB} = 20 \log_{10} G$$

Bode Plot  
cut-off frequency  $\omega_c$ .
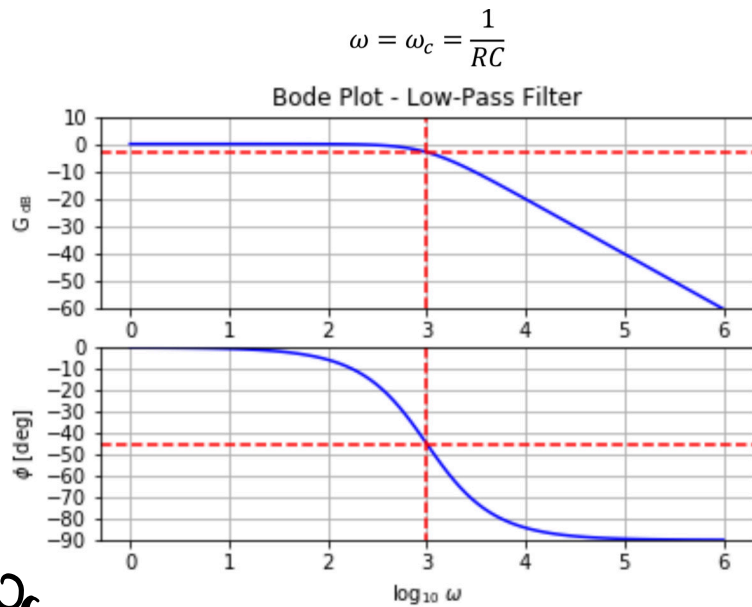
$$\omega_c = \frac{1}{RC} = \frac{1}{\tau}$$



$$g_{dB} = -3$$

or

$$g = \frac{1}{\sqrt{2}}$$

$$\phi = -45^\circ$$


or

$$\phi = -\frac{\pi}{4} \text{ rad}$$

for frequencies  $\omega \ll \omega_c$ , are passed through the filter. pass band  $\leftarrow$   $\vdots$   $\rightarrow$  stop band

for frequencies  $\omega \gg \omega_c$ , are stopped by the filter.

### High-Pass LC Filter

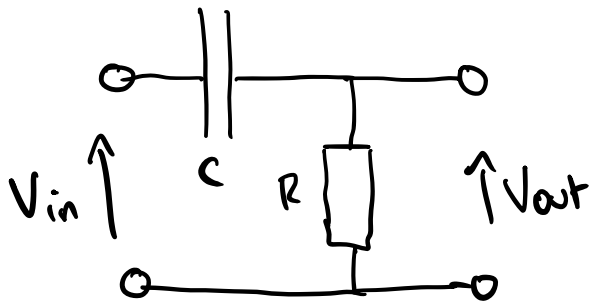


take the output across the resistor.

$$G = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} \quad \tan \phi = \frac{1}{\omega RC}$$

$$\omega_c = \frac{1}{RC}$$

for frequencies below the cut-off frequency, the gain tends to zero. for frequencies above the cut off frequency, the gain tends to 1.

### High-Pass RL Filter

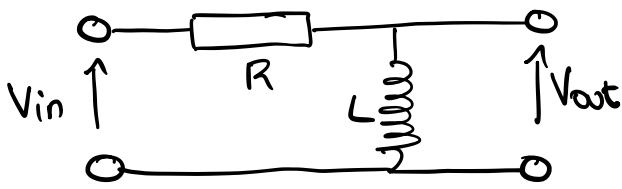

$$\tan \phi = \frac{\omega_c}{\omega} \quad \omega_c = \frac{R}{L}$$

$$G = \frac{\omega/\omega_c}{\sqrt{1 + (\omega/\omega_c)^2}}$$

When  $\omega_0 = \frac{1}{RC}$ , this takes the form of the RC filter.

$$Z_C \propto \frac{1}{\omega}$$

$$Z_L \propto \omega$$

you can swap the resistor and inductor to get a low pass filter.

