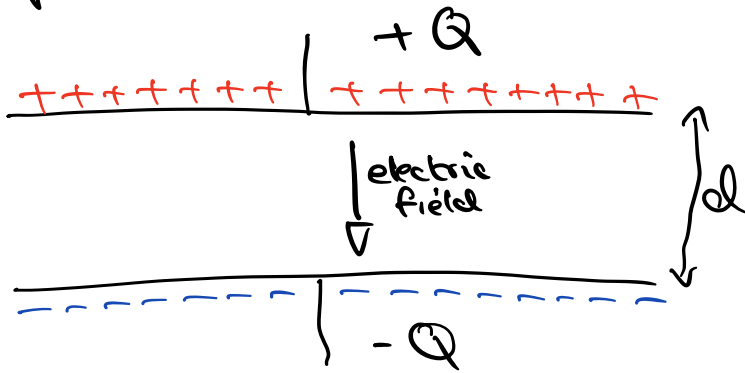


Capacitance



electric field strength

$$E = \frac{V}{d}$$

change in voltage

distance

$$C = \frac{Q}{V}$$

charge

voltage

capacitance

In a parallel plate capacitor

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

A = area (m^2)

ϵ_0 = permittivity of free space (F/m)


ϵ_r = relative permittivity

C = capacitance

ϵ_r is also called the dielectric constant.

Equivalent Capacitance

Parallel

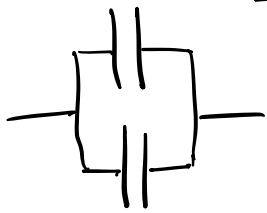

$$C_T = C_1 + C_2$$

Series



$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$

Energy stored

$$U = \frac{CV^2}{2} = \frac{Q^2}{2C}$$

$$(Q = CV)$$

during the charging process: $q = Cv$. to increase charge from q to $q + dq$: $dw = v dq = \frac{q}{C} dq$

$$\frac{dw}{dq} = \frac{q}{C} = v$$

As charge is conserved, a capacitor is always overall neutral. ($+Q - Q = 0$)

Current/Voltage Relationship

$$q = Cv$$
$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$


N.B.

CAPITALS = constant
lower-case = variable

NO charge moves between the plates (the dielectric is an insulator). All charges move through the voltage source (eg. battery).

RC circuit

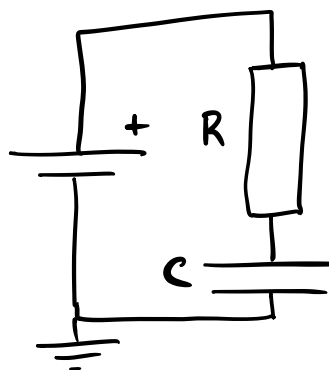the voltage source is switched on at time $t = 0$.



Charging the Capacitor:

$$E = iR + \frac{q}{C} \quad \leftarrow \text{Kirchoff's voltage law}$$

$$E = R \frac{dq}{dt} + \frac{1}{C} q$$

$$EC = RC \frac{dq}{dt} + q$$


$$EC - q = RC \frac{dq}{dt}$$

$$\frac{dq}{EC - q} = \frac{dt}{RC}$$

\Rightarrow

$$\int_0^q \frac{dq'}{q' - EC} = \int_0^t \frac{-dt'}{RC}$$
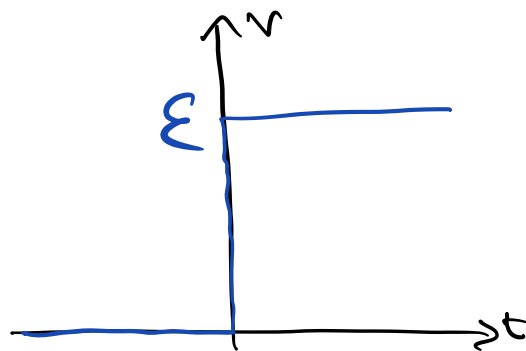
$$\Rightarrow \left[\ln(q - EC) \right]_0^q = \left[\frac{-t}{RC} \right]_0^t \Rightarrow \ln \left[\frac{q - EC}{-EC} \right] = \frac{-t}{RC}$$



$$\frac{q - \mathcal{E}C}{\mathcal{E}C} = e^{-\frac{t}{RC}} \Rightarrow q = \mathcal{E}C(1 - e^{-t/RC})$$

Similarly for current: $i = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}}$

and for voltage:

$$V_C = \mathcal{E}(1 - e^{-\frac{t}{RC}})$$


← across the capacitor

$$V_R = \mathcal{E}e^{-\frac{t}{RC}}$$

← across the resistor

τ is the time constant. $\tau = RC$ (units = seconds). It is the time taken for something to fall by a factor of $e^{-1} \approx 37\%$.

Discharging a Capacitor:

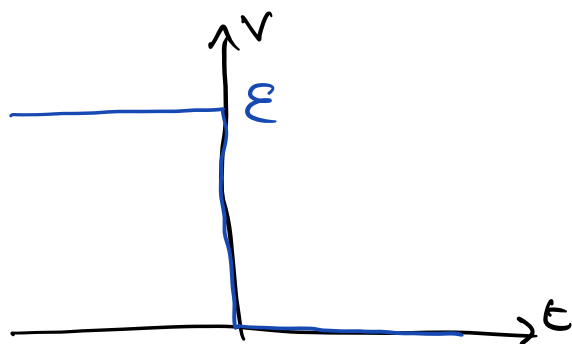

$$\begin{aligned} 0 &= V_C + V_R = iR + \frac{q}{C} \\ &= R \frac{dq}{dt} + \frac{1}{C}q = RC \frac{dq}{dt} + q \\ \Rightarrow \int_0^t -\frac{1}{RC} dt' &= \int_0^q \frac{dq'}{q'} \end{aligned}$$

$$\left[-\frac{t}{RC}\right]_0^t = \left[\ln(q')\right]_{C\mathcal{E}}^q \Rightarrow \frac{-t}{RC} = \ln\left[\frac{q}{C\mathcal{E}}\right] \Rightarrow q = C\mathcal{E}e^{-\frac{t}{RC}}$$

for current: $i = -\frac{\mathcal{E}}{R} e^{-t/RC}$

$$P_R = V_R i = i^2 R$$

$$V_R = -\mathcal{E}e^{-t/RC} \quad \text{positive power} = \mathcal{E}e^{-t/RC}$$

← resistor dissipating

← capacitor voltage

Energy & Power Charging

$$P_R = V_R i = i^2 R$$




- positive power
- resistor dissipating

$$P_C = V_C i$$

- positive power
- capacitor storing energy

$$P_S = -V_S i = -\mathcal{E} i$$

- negative
- source providing energy

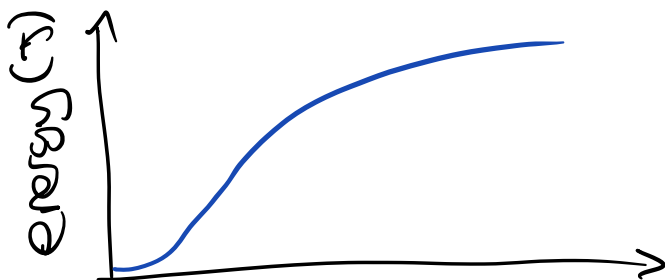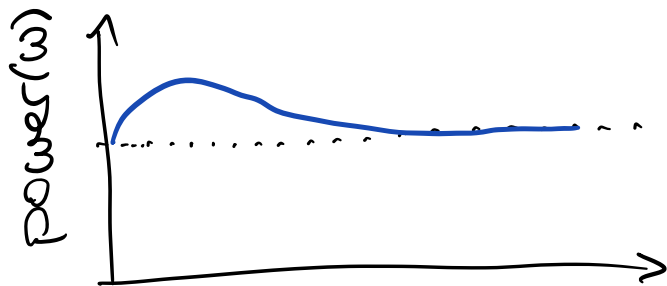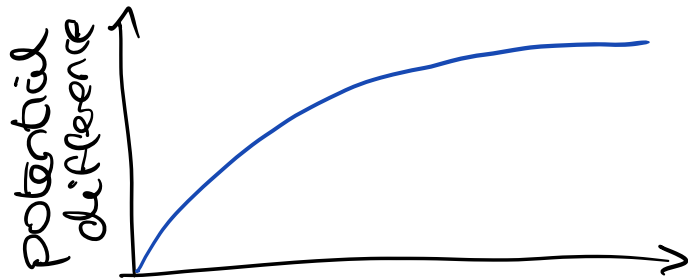

Discharging

$$P_R = V_R i = i^2 R$$

- positive power
- resistor dissipating

$$P_C = V_C i$$

- negative
- realising stored energy

$$P_S = -V_S i = 0$$

- no source power

$$\sum P_n = 0$$

