

Alternating Current


$$V(t) = A \cos(\omega t + \phi)$$

amplitude ↗

$$V_{pp} = 2A$$

$$V_{RMS} = \frac{A}{\sqrt{2}}$$

$$RMS = \sqrt{\langle V^2 \rangle}$$

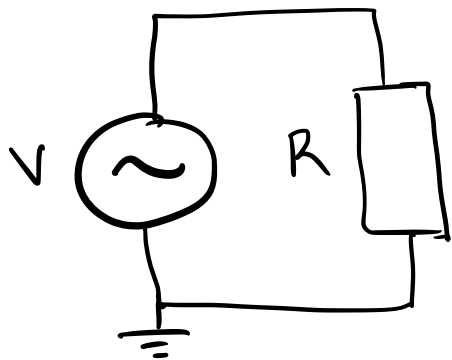

$$V = V_0 \cos(\omega t)$$

$$i = \frac{V_0}{R} \cos(\omega t)$$

$$P_R = Vi = \frac{V_0^2}{R} \cos(\omega t)$$

$$\langle P_R \rangle = \frac{V_0^2}{2R}$$

$$P_{avg} = V_{RMS} I_{RMS} \cos(\phi)$$

Phase difference between V & I .

$$\uparrow \frac{V_0}{\sqrt{2}}$$


$$\uparrow \frac{I_0}{\sqrt{2}} = \frac{V_0}{R\sqrt{2}}$$

$$V = V_0 \cos(\omega t)$$

$$i = C \frac{dV}{dt}$$

$$= -\omega C V_0 \sin(\omega t)$$
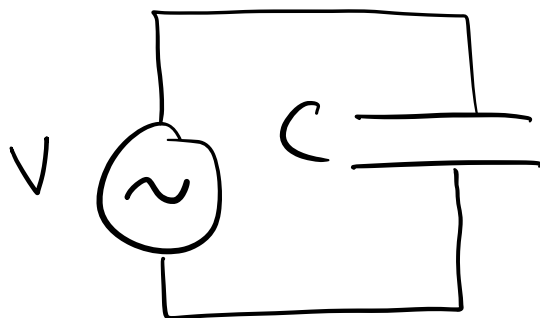
$$= \omega C V_0 \cos(\omega t + \pi/2)$$



Current $\pi/2$ rads out of phase with the voltage

$$P_{avg} = V_{RMS} I_{RMS} \cos \phi = 0$$

$$P_c = Vi = V_0 \cos(\omega t) \omega C V_0 \cos(\omega t + \pi/2)$$

$$= -\omega C V_0^2 \cos(\omega t) \sin(\omega t) = -\frac{1}{2} \omega C V_0^2 \sin(2\omega t)$$

$$\langle P_c \rangle = 0$$


Driven LCR circuit

$$V_S = V_R + V_L + V_C$$

$$V_0 \cos(\omega t) = Ri + L \frac{di}{dt} + \frac{1}{C} q$$

$$\frac{V_0}{L} \cos(\omega t) = \frac{d^2 q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q$$
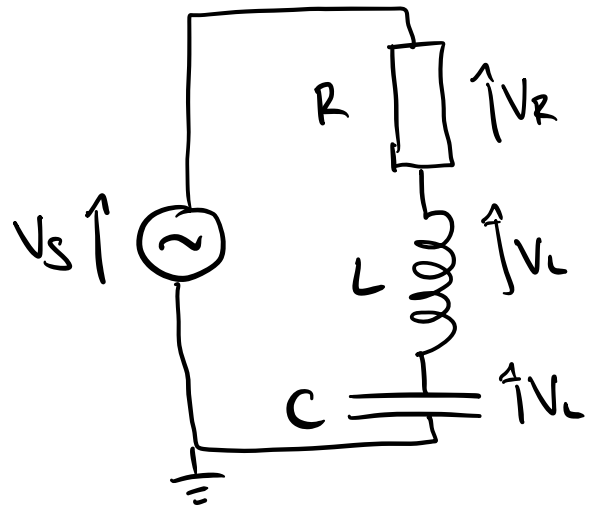
$$\frac{V_0}{L} \cos(\omega t) = \ddot{q} + \gamma \dot{q} + \omega_0^2 q \quad \gamma = \frac{R}{L} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$



let q be complex \tilde{q} .

$$\ddot{\tilde{q}} + \gamma \dot{\tilde{q}} + \omega_0^2 \tilde{q} = \frac{V_0}{L} e^{j\omega t}$$

complex
constant
CAPITAL

$$\tilde{q} = \tilde{Q} e^{j\omega t}$$

$$\tilde{Q} = \frac{V_0/L}{\omega_0^2 - \omega^2 + j\omega\gamma}$$

from complex
analysis course

in electronics
we use j instead
of i to be $\sqrt{-1}$.

$$\text{Amplitude of Oscillation} = |\tilde{Q}|$$

$$\text{Phase of Oscillation} = \arg(\tilde{Q})$$

absolute
value


Our steady-state solution is

$$q(t) = \text{Re}(\tilde{q}) = |\tilde{Q}| \cos(\omega t + \arg(\tilde{Q}))$$

see complex
analysis

$$q(t) = \frac{V_0/L}{\sqrt{(\omega_0^2 - \omega^2)^2 + \omega^2 \gamma^2}} \cos(\omega t + \phi)$$
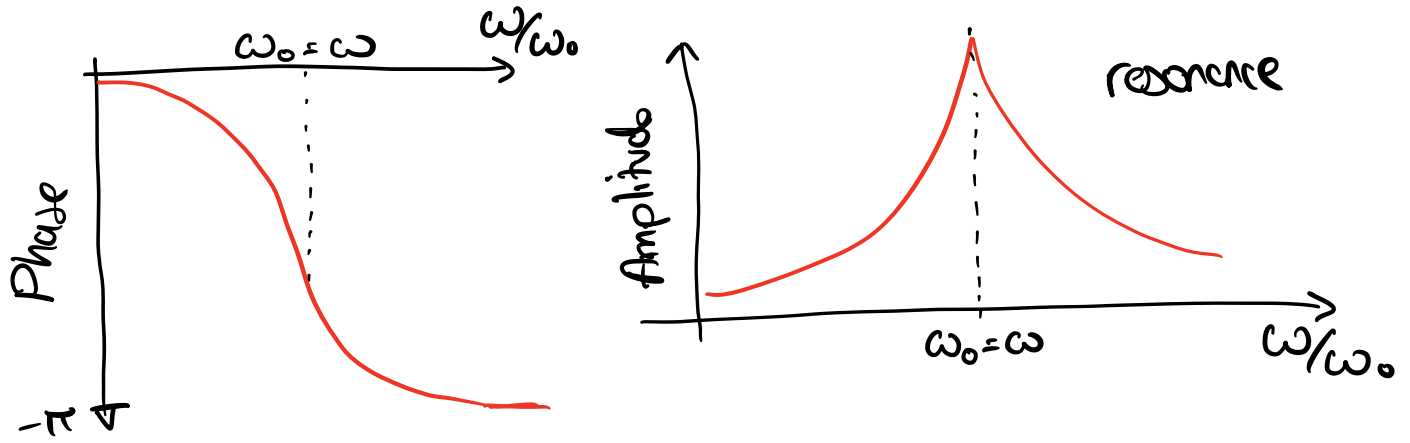
$$\tan \phi = \frac{-\omega \gamma}{\omega_0^2 - \omega^2}$$



Phasors


We can represent any oscillating signal using complex quantities.

$\tilde{q} = \tilde{Q} e^{j\omega t}$ $\tilde{q} = Q e^{j(\omega t + \phi)} = Q e^{j\phi} e^{j\omega t}$
 \tilde{Q} is the phasor such that $|\tilde{Q}|$ is the amplitude & $\arg(\tilde{Q})$ is the phase. $\tilde{Q} = Q e^{j\phi} \leftarrow \text{phasor}$

Kirchoff's voltage law works for complex numbers too.

$$\tilde{V}_S = \tilde{V}_L + \tilde{V}_C + \tilde{V}_R$$

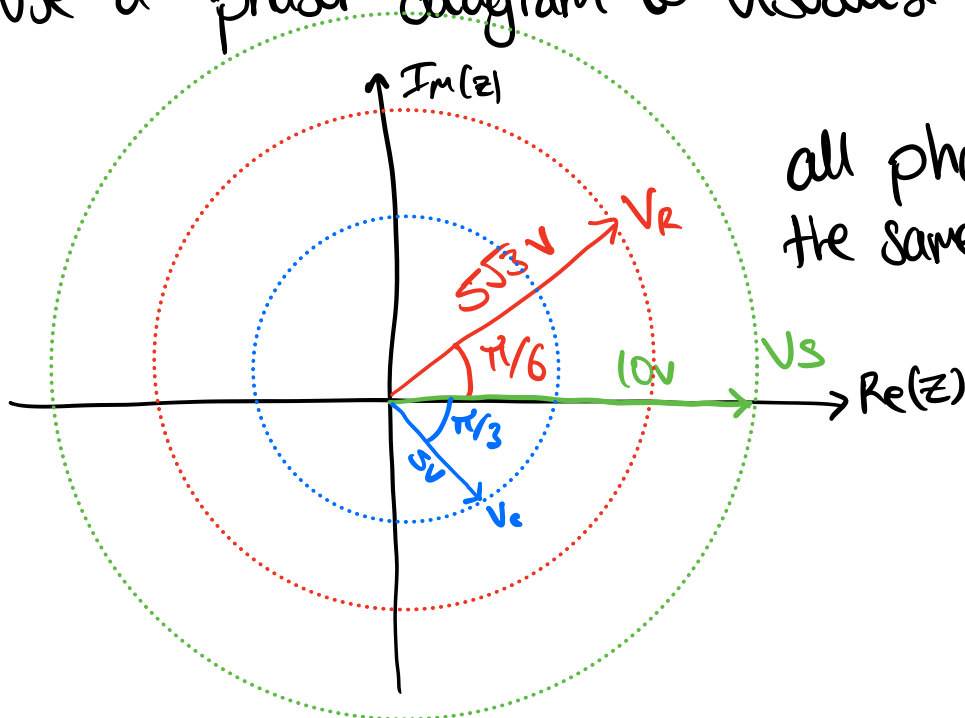We can use a phasor diagram to visualise our phasors:



all phasors have the same angular frequency.