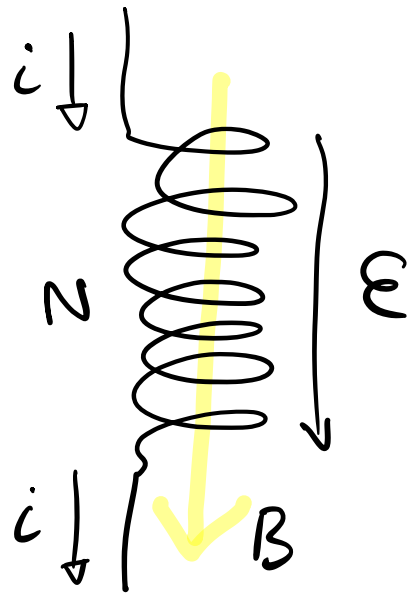


# Inductance

A cylindrical coil of  $N$  turns with current  $i$ .

It stores energy in a magnetic field when electric current flows through it.

When the current flowing through the coil changes, the time-varying magnetic field induces an **electromotive force** (e.m.f.) (voltage) in the conductor, described by **Faraday's law of induction**. According to **Lenz's law**, the induced voltage has a polarity (direction) which opposes the change in current that created it. As a result, inductors oppose any changes in current through them.



induced EMF  $\rightarrow \mathcal{E} = -N \frac{d\Phi}{dt}$   $\leftarrow$  magnetic flux


Lenz's law  $\rightarrow$  number of coils

The magnetic flux can be found by:

permeability of free space  $\rightarrow$  relative permeability  $\rightarrow$  number of coils  $\rightarrow$  current

magnetic flux  $\rightarrow \Phi = BA = \frac{\mu_0 \mu_r N^2 A i}{d}$

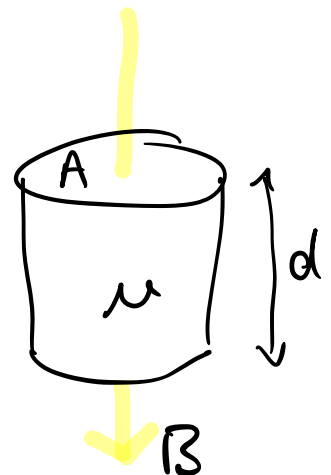magnetic field strength  $\rightarrow$  cross sectional area  $\rightarrow$



It is often easier to use the inductance ( $L$ ) instead of the magnetic field.

induced EMF  $\rightarrow \mathcal{E} = -L \frac{di}{dt}$   $\leftarrow$  current

$\rightarrow$  inductance

inductance can be found by:

$$L = \frac{\mu_0 \mu_r N^2 A}{d}$$


# Equivalent Inductance

## Series



$$L_{eq} = L_1 + L_2 + \dots$$

## Parallel

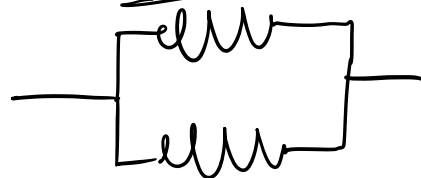



$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots$$

## Current & Voltage


from KVL:  $\mathcal{E}_s + \mathcal{E}_L = 0$

$$V_L + \mathcal{E}_L = 0$$


$$V_L = L \frac{di}{dt}$$

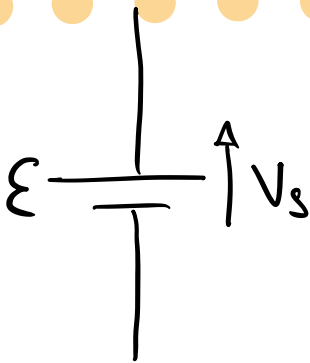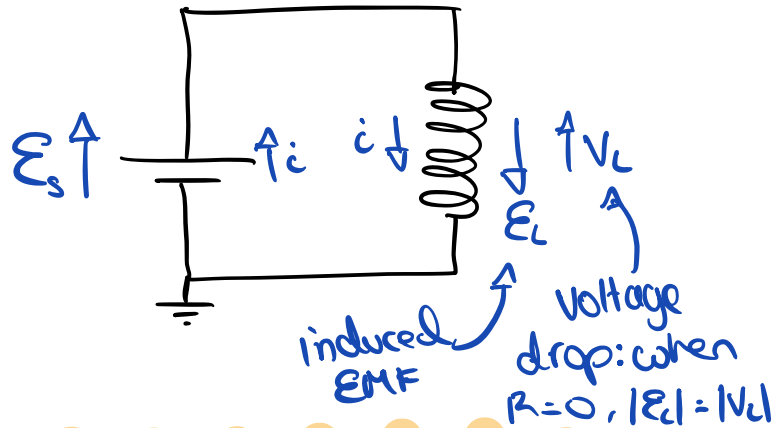


$$V_s = \mathcal{E}$$

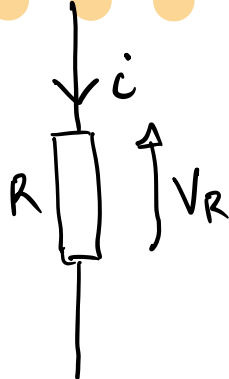

$$V_R = iR$$

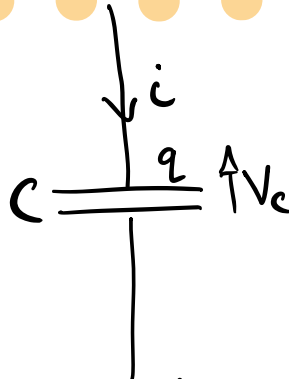

$$i = C \frac{dV_C}{dt}$$

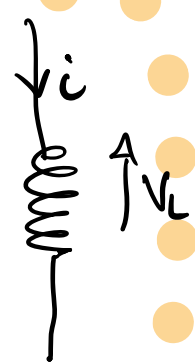

$$V_L = L \frac{di}{dt}$$

## Energy stored

inductance  $\rightarrow$   $U = \frac{L I^2}{2}$   $\leftarrow$  current

energy stored  $\rightarrow$

$$\frac{dU}{dt} = V_L i = L i \frac{di}{dt}$$

$$dU = L i di$$


$$\int_0^U dU = \int_0^I L i di$$

$$U = \frac{L i^2}{2}$$

## RL circuit

Energising:

Source is switched on at time  $t=0$ .

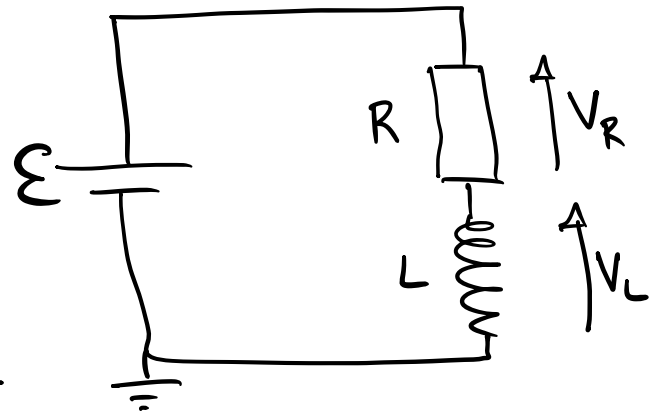

$$\mathcal{E} = Ri + L \frac{di}{dt}$$

time const.  
↙

$$\mathcal{E} = V_R + V_L$$

$$i = \frac{\mathcal{E}}{R} \left[ 1 - e^{-\frac{tR}{L}} \right] \quad \tau = \frac{L}{R}$$

$$V_R = iR = \mathcal{E} \left[ 1 - e^{-\frac{tR}{L}} \right]$$

$$V_L = L \frac{di}{dt} = \mathcal{E} e^{-\frac{tR}{L}}$$

De-energising:

$$0 = Ri + L \frac{di}{dt} \Rightarrow i = \frac{\mathcal{E}}{R} e^{-\frac{tR}{L}}$$

$$V_R = iR = \mathcal{E} e^{-\frac{tR}{L}}$$

$$V_L = L \frac{di}{dt} = -\mathcal{E} e^{-\frac{tR}{L}}$$

## Power

### Energising

$$\square P_R = V_R i = i^2 R$$

positive power

dissipating energy

$$\square P_L = V_L i$$

positive power

storing energy

$$\square P_S = -V_S i = \mathcal{E} i$$

negative power

releasing energy

### De-Energising

$$\square P_R = V_R i = i^2 R$$

positive power

$$\square P_L = V_L i$$

negative power


releasing stored energy

$$\square P_S = -V_S i = 0$$

no source power

$$P_S + P_L + P_R = 0$$

LC circuit  
for  $t > 0$ ,

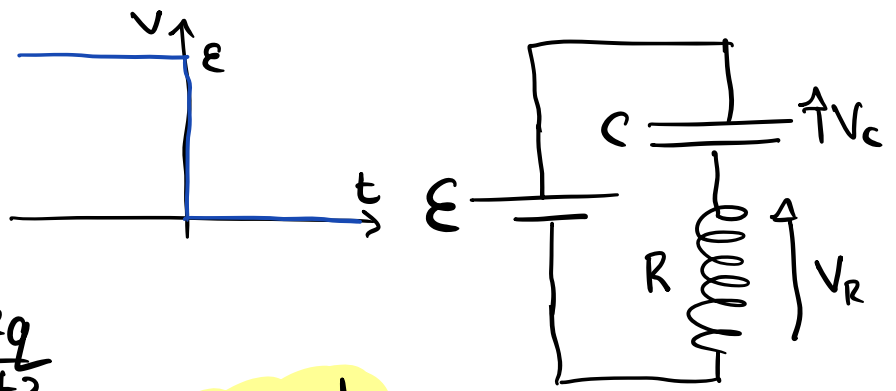

$$0 = Cq + L \frac{d^2q}{dt^2}$$


$$q = -\frac{1}{LC} \ddot{q}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$q_0 = C\mathcal{E}$$

$$\mathcal{E} = L \frac{di}{dt} = L \frac{dq}{dt}$$

$$q = q_0 \cos(\omega_0 t)$$

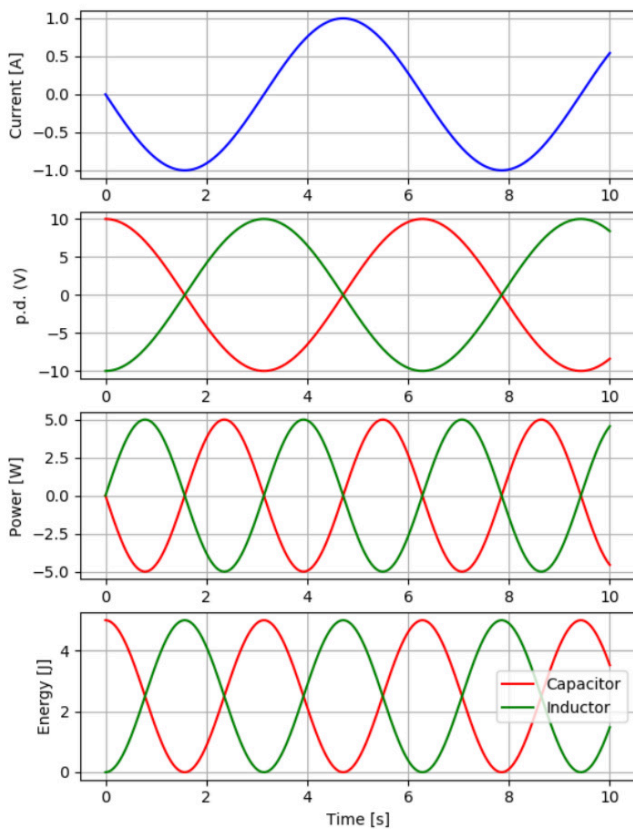

✱ the p.d. for the capacitor is in antiphase with the p.d. for the inductor.